

 


 

Analog Lab project (EE254)


 



Design a D-flip flop using transistors.

Group -15



Members

Advait Varma	230002006
Himanshu	230002029
Praneet Masiya	230002055
David Kumar	230002022
Yash Shrivastava	230002067

  



 



Introduction

  



What is a D flip flop

   A D flip-flop, also known as a D-type or data flip-flop, is a digital storage element utilized in sequential logic circuits. It captures the value of the D (data) input at a specific part of the clock cycle, typically on the rising or falling edge of the clock signal, and holds this value until the next clock event. Hence, they are also known as Delay Flip Flop






 





Context

  

Difference between A latch and a Flip Flop

  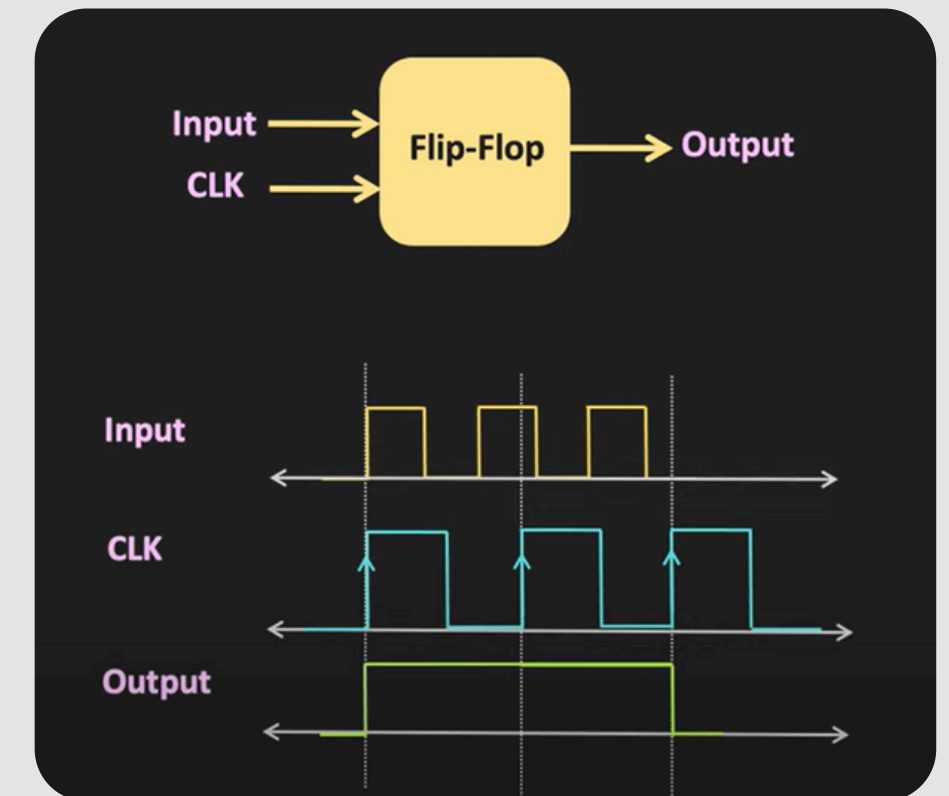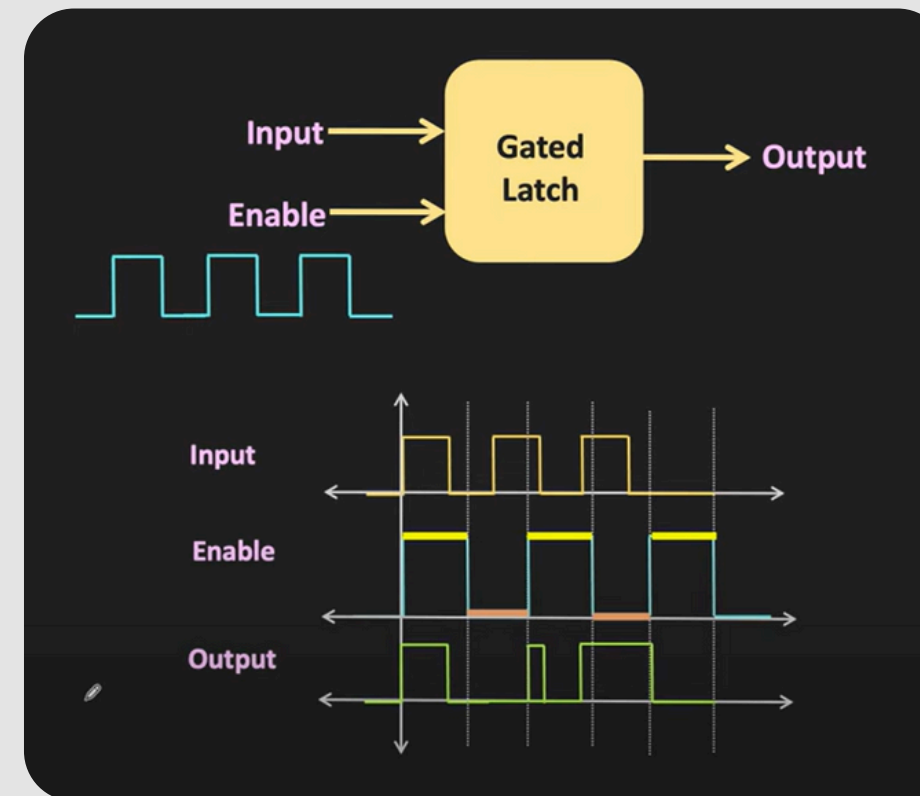The key difference between a latch and a flip-flop lies in their triggering mechanism: latches are level-triggered, responding to the continuous presence of input signals, while flip-flops are edge-triggered, responding only to changes (edges) of a clock signal.



   



Process


First We Made The Ideation That we Need to Make The logic gates First
The use of Components was too heavy
And we Didn't want to rely on that
Around 9-10 BJTs was required.

So we looked For a more optimized Approach , we considered creating the Flip flop using only Few BJTs, By Creating A basic SR latch.




Then We Divided The Project into 2 parts

  - Making D FlipFlop
- Making Astable Multivibrator using OP-AMP




 



Phases Of our Project

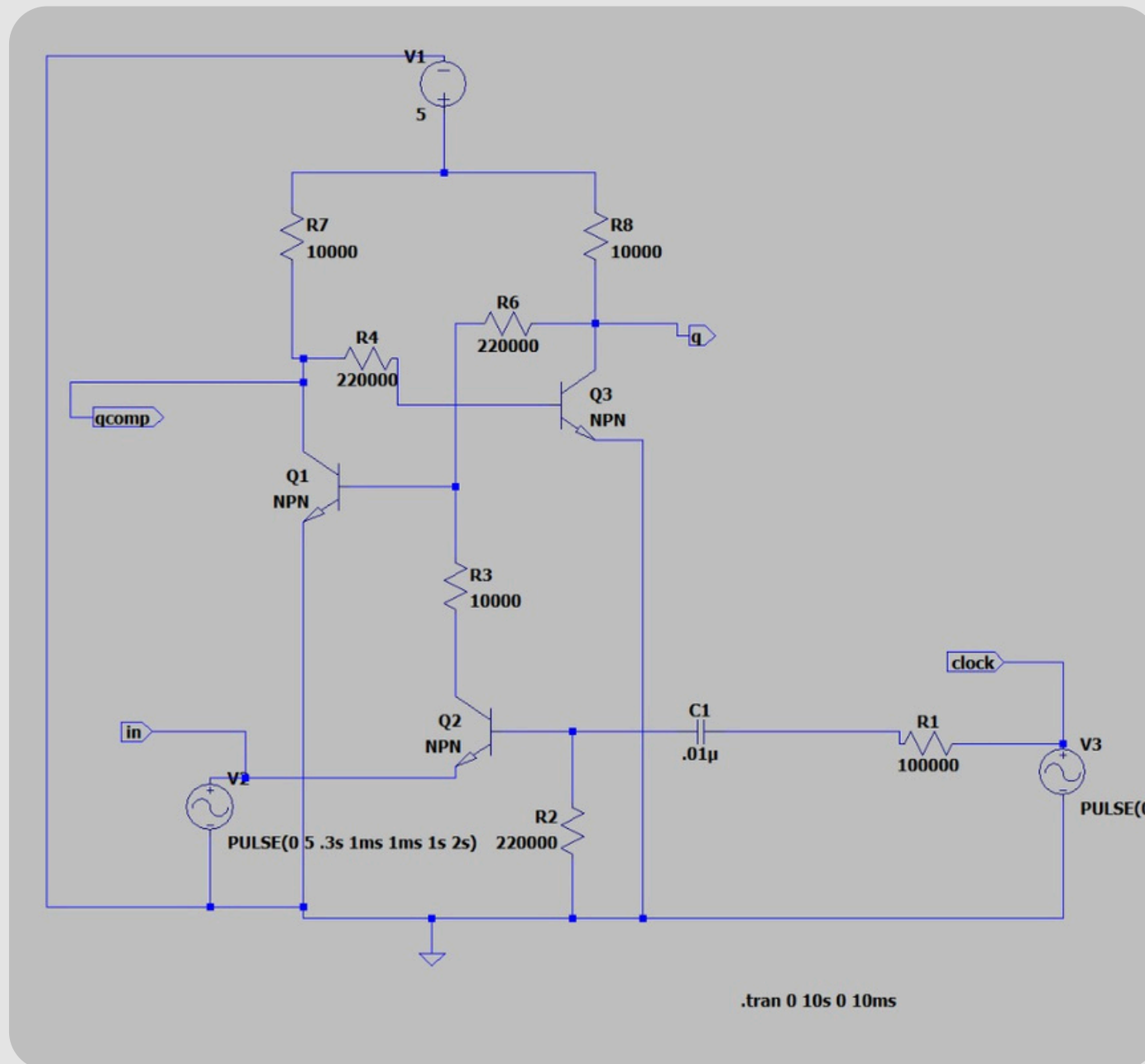  

D flip Flop

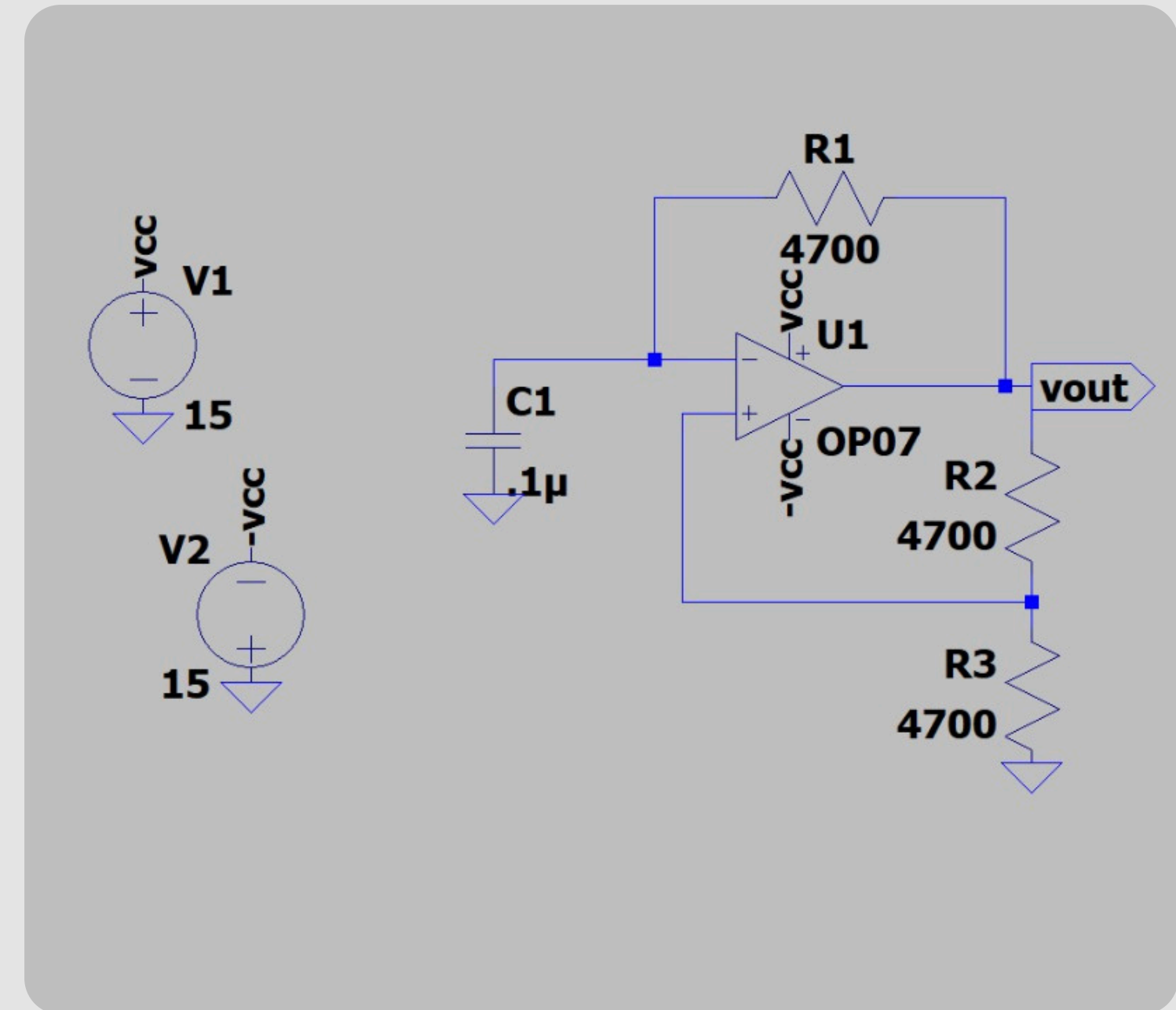


Astable MultiVibrator


 
 


D flip Flop


Here Instead of making Logic gates One by one and then Implementing the gates , We designed The flip Flop Only by using 3 BJTs (NPN). It operates By using the BJT in saturation Region
I.e Gates Were Not Necessary

D	CLK	Q	Q'
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

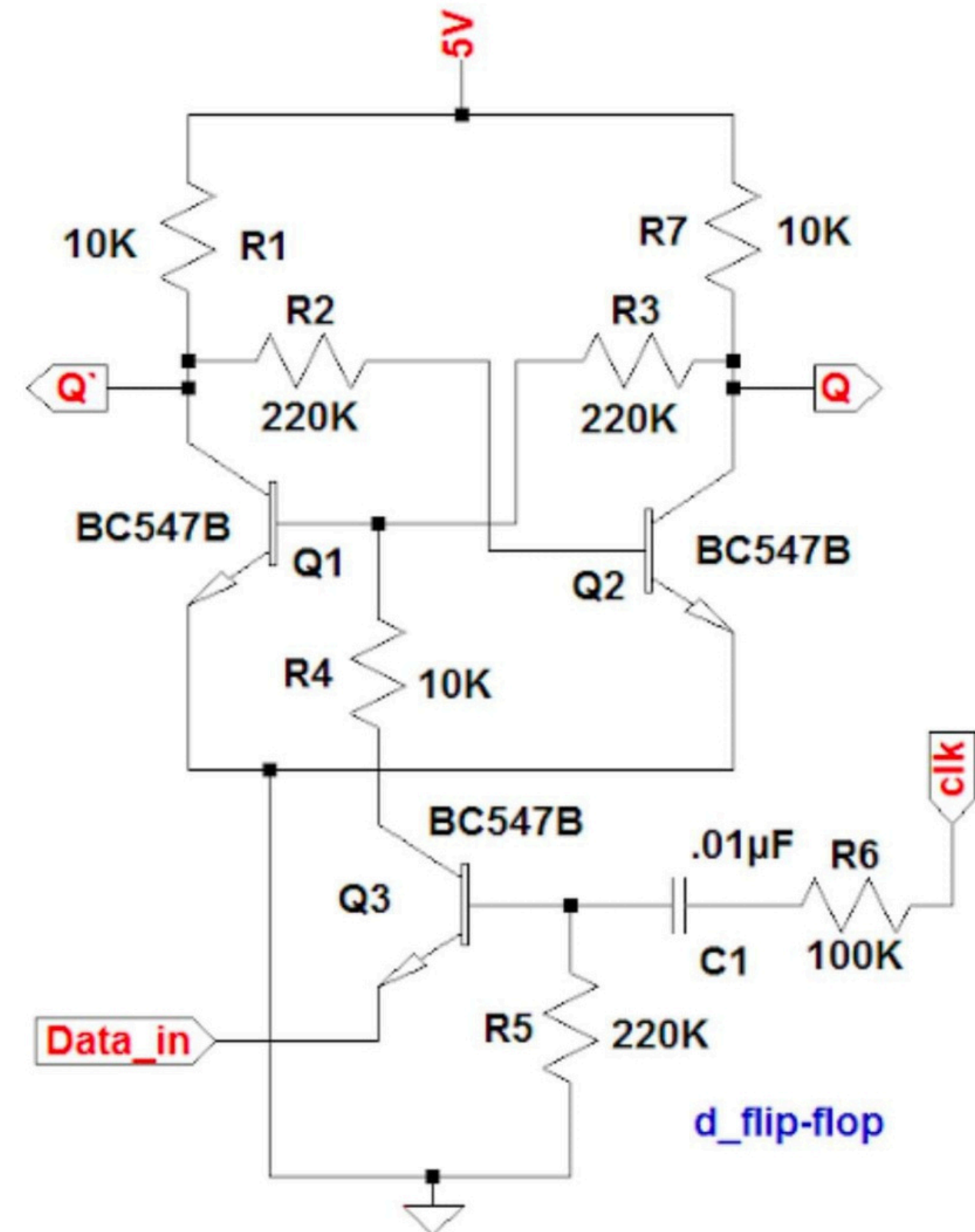


   

D flip Flop

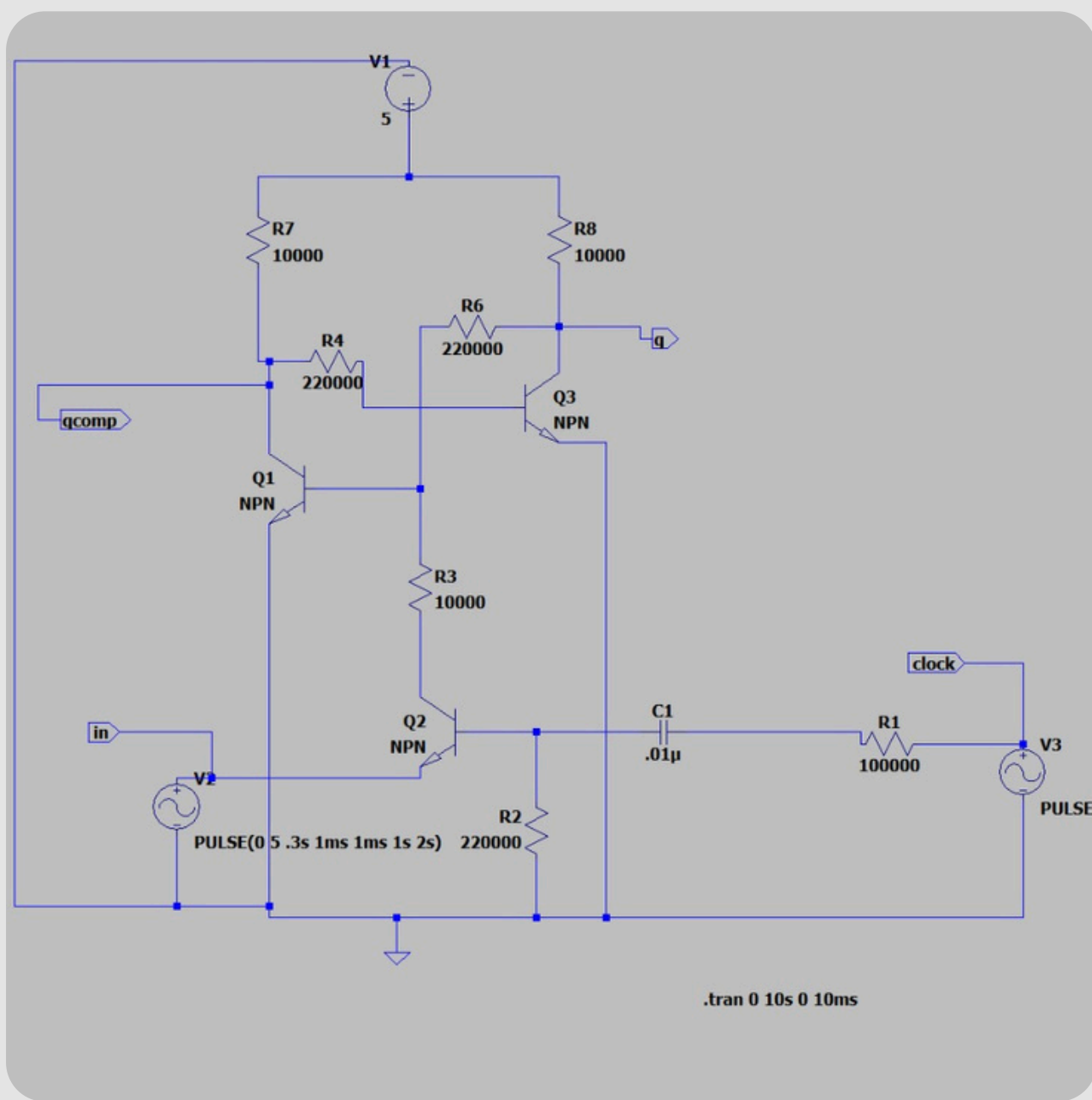



Schematic

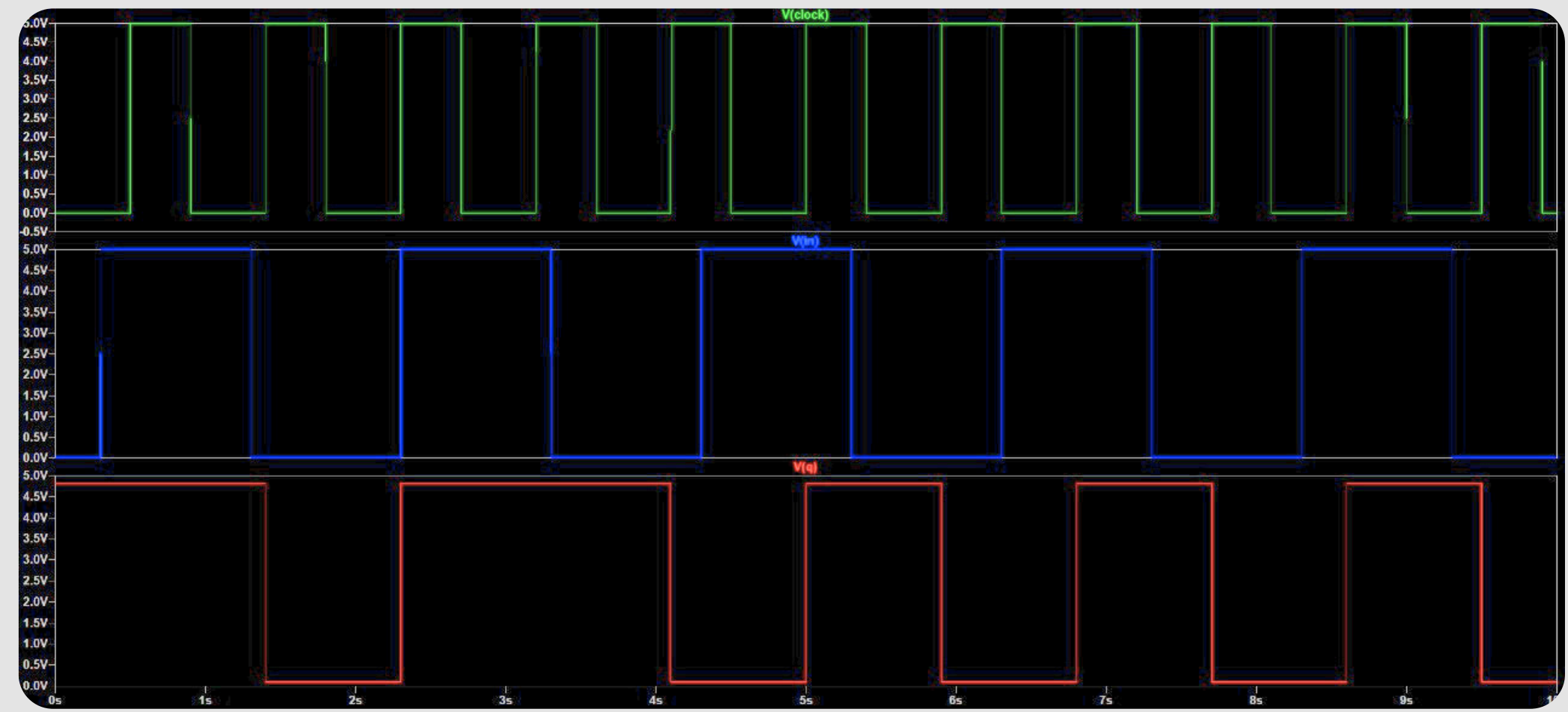



Output

Green : clk
Blue : Vin
Red : Vout

 



 


Astable Multivibrator


 
 


An astable multivibrator, also called a free-running multivibrator, is a circuit that continuously produces square waves or pulses without the use of an external trigger. The term “astable” refers to the absence of a stable state in this particular type of multivibrator.

  
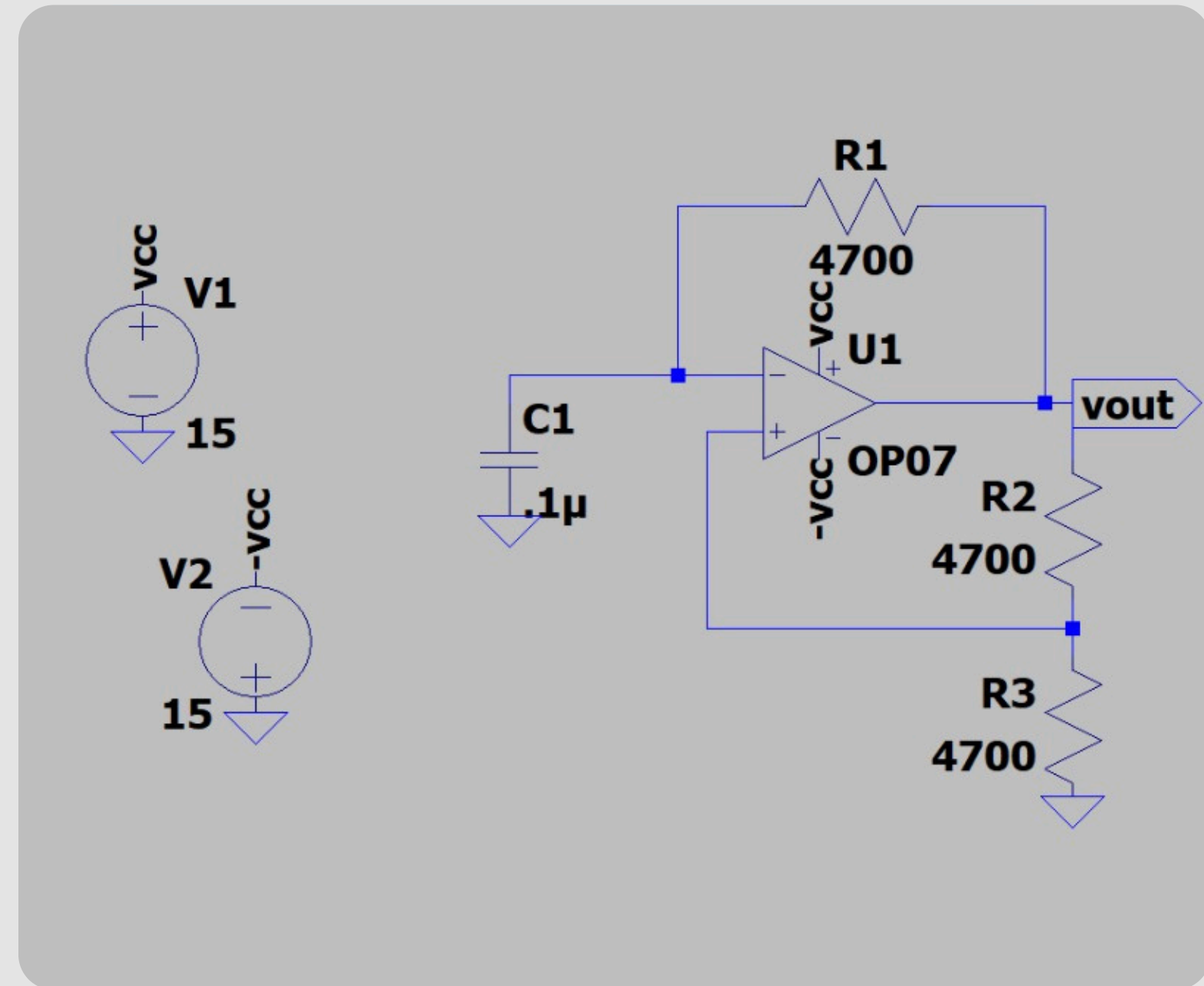
$$T = 2\tau \ln \frac{1 + \beta}{1 - \beta}$$





  
 



Astable Multivibrator

 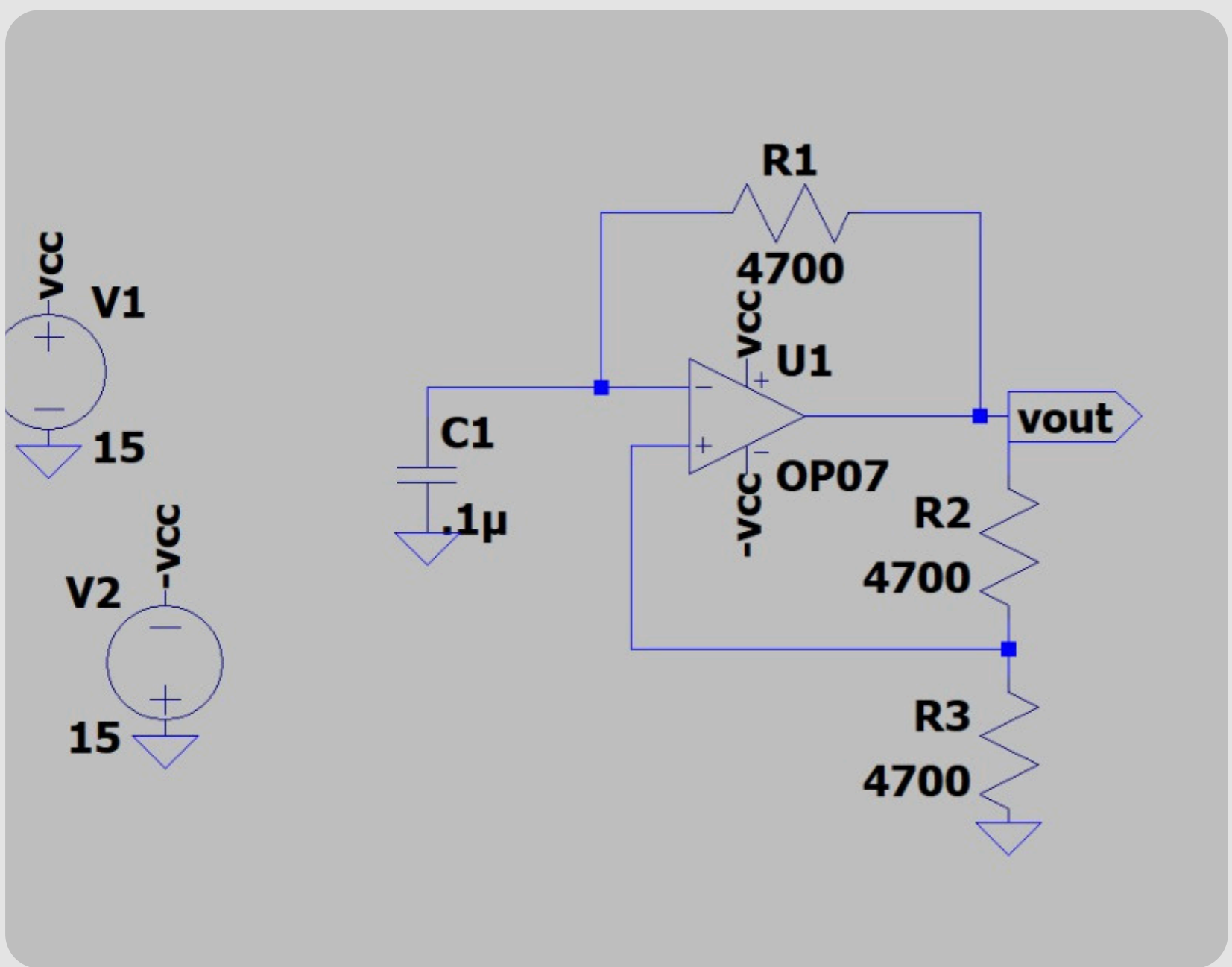






Output

Schematic

  

 


Final Circuit

     




 
PROBLEMS FACED

WHEN IMPLEMENTING USING 4 GATES
WE NEEDED 11 BJTS WHICH OPENED A
LOT OF SPACE FOR ERRORS
ALSO IT WAS NOT EFFICIENT AND FAST

WE FIRST USED ASTABLE
MULTIVIBRATOR USING BJT FOR CLOCK
SIGNAL , BUT WE GOT LOWER
AMPLITUDE , SAME FOR FREQUENCY .
THIS OCCURED DUE TO VALUE OF R&C







Results

    

The following circuit uses an astable multivibrator to generate the clock signal needed to drive the D flip-flop and produce the desired output. Initially, we built the astable multivibrator using BJTs (Bipolar Junction Transistors). However, during testing, we found that the output amplitude was low, and the frequency was also not stable.

 To solve these issues, we replaced the BJT-based multivibrator with an Op-Amp-based multivibrator. Using the Op-Amp improved both the amplitude and the frequency stability of the clock signal, thereby enhancing the performance of the D flip-flop circuit.



   

Thank You

